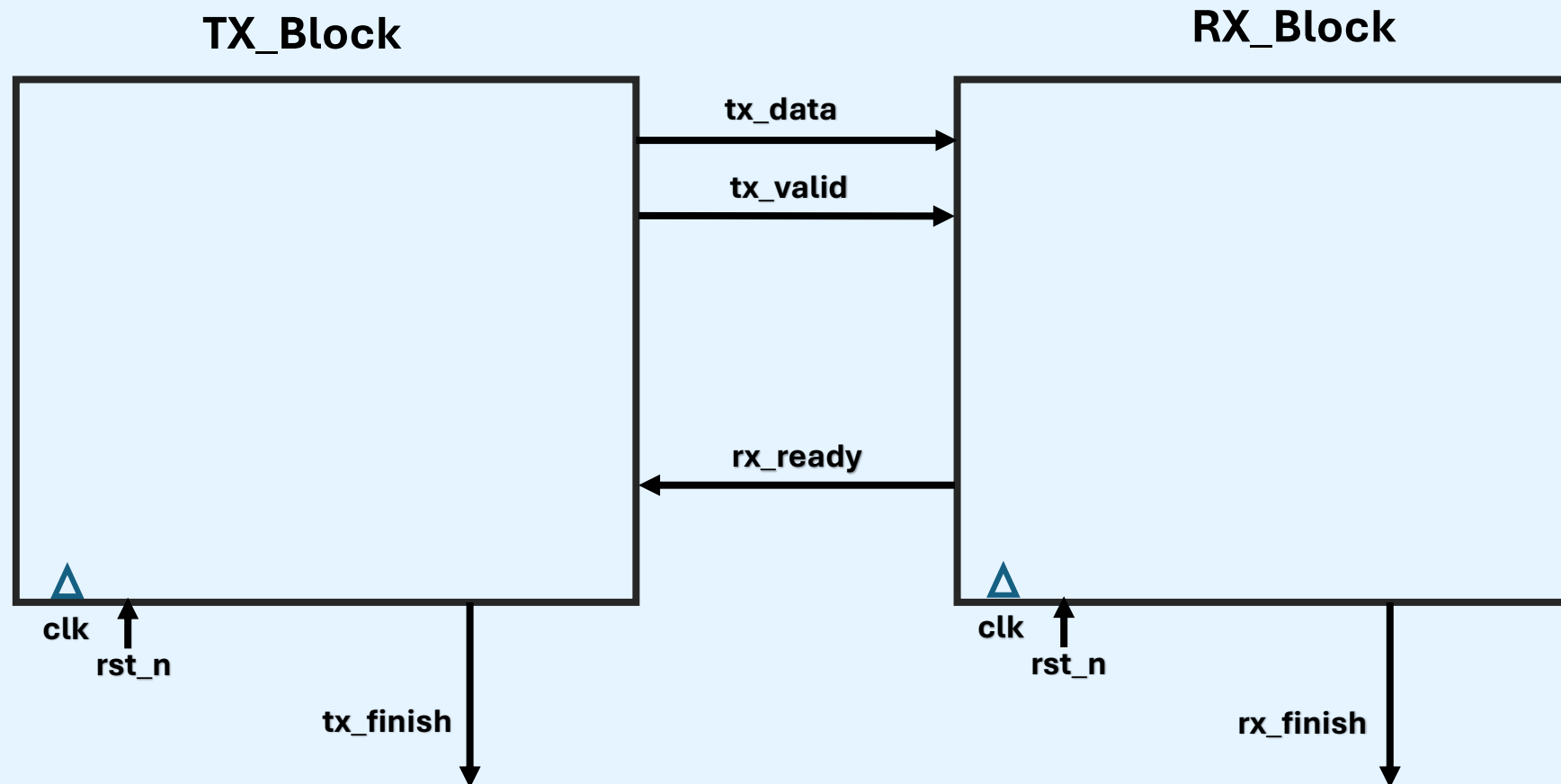



Project

Serial Communication




Project

Waveform

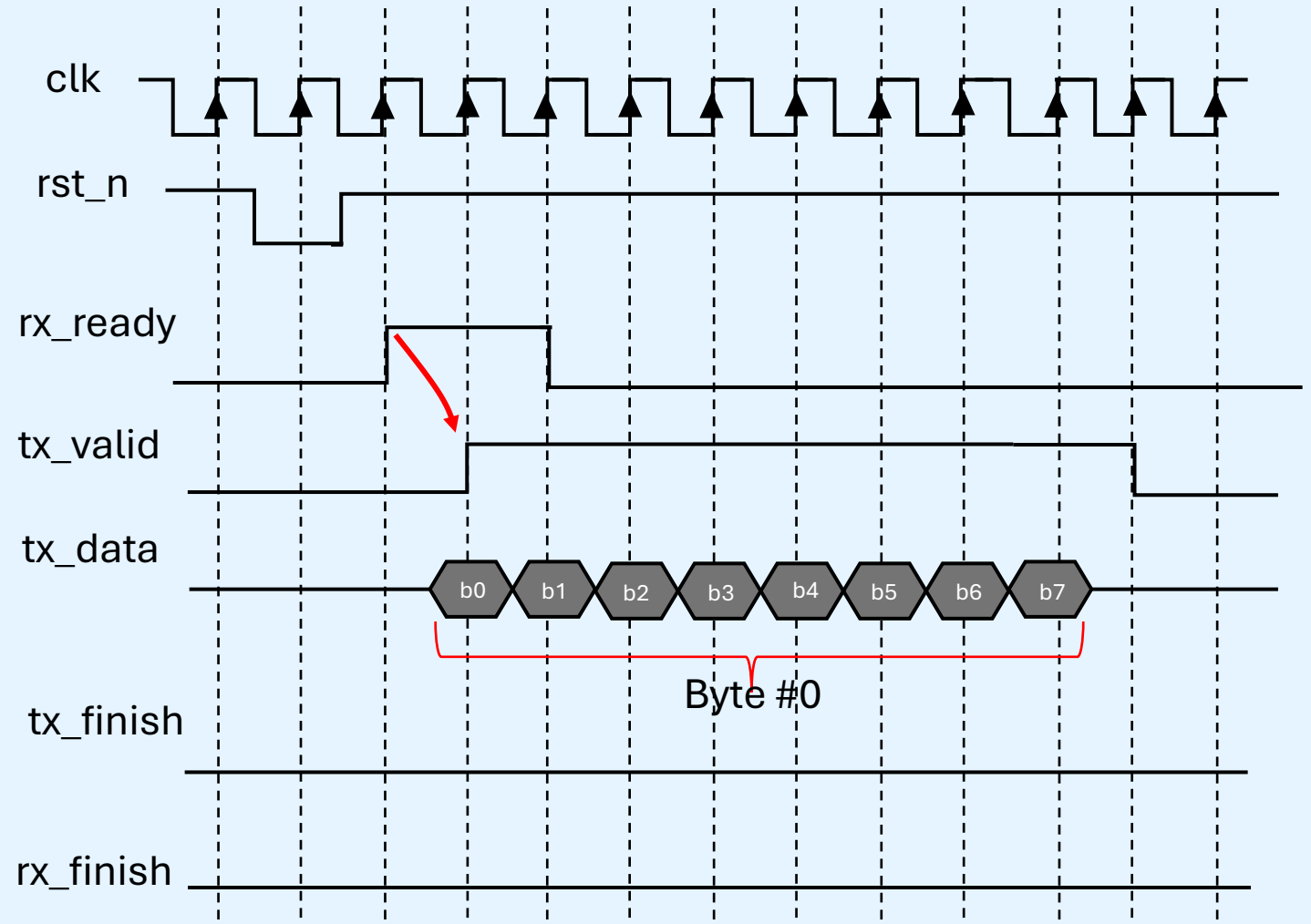

Project


Waveform

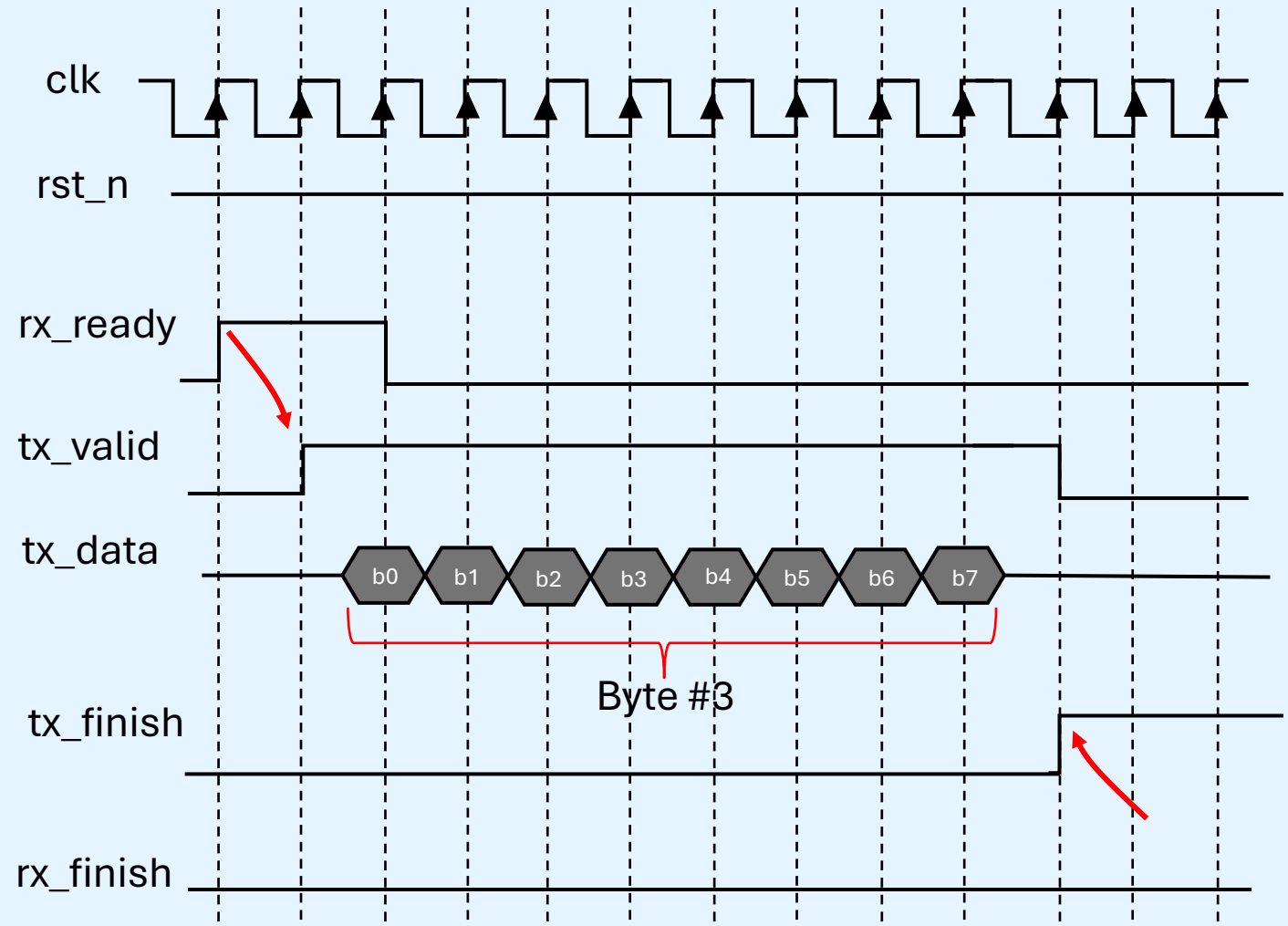



TX Block


I/O definition

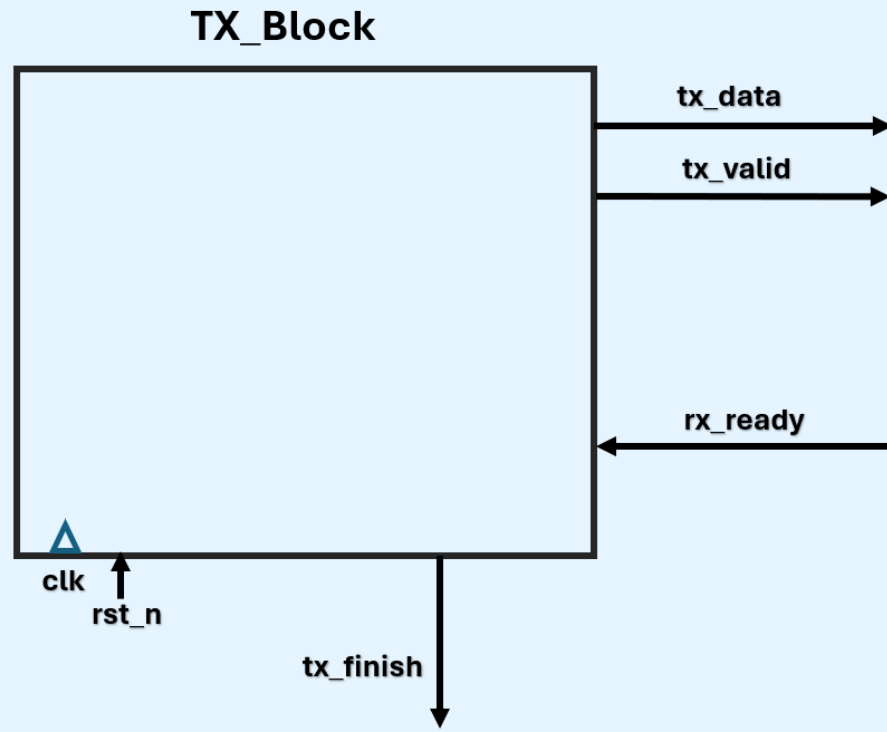

name	I/O	Description
clk	I	50MHz
rst_n	I	active-low
rx_ready	I	Rx block is ready to receive data
tx_valid	O	Data on the tx_data wire is valid
tx_data	O	Serial data
tx_finish	O	All data is sent


TX Block

Architecture

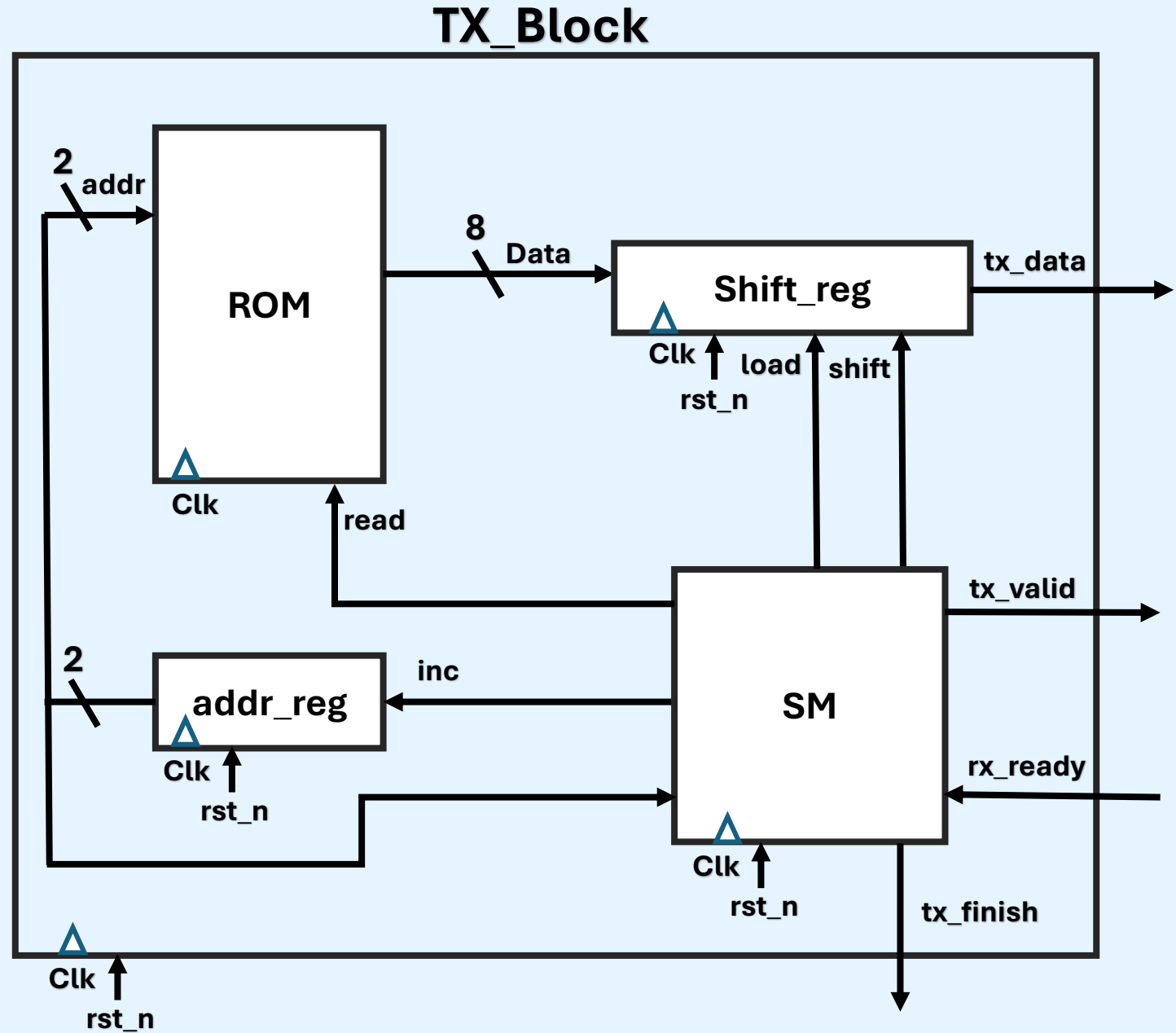


TX Block

State Machine

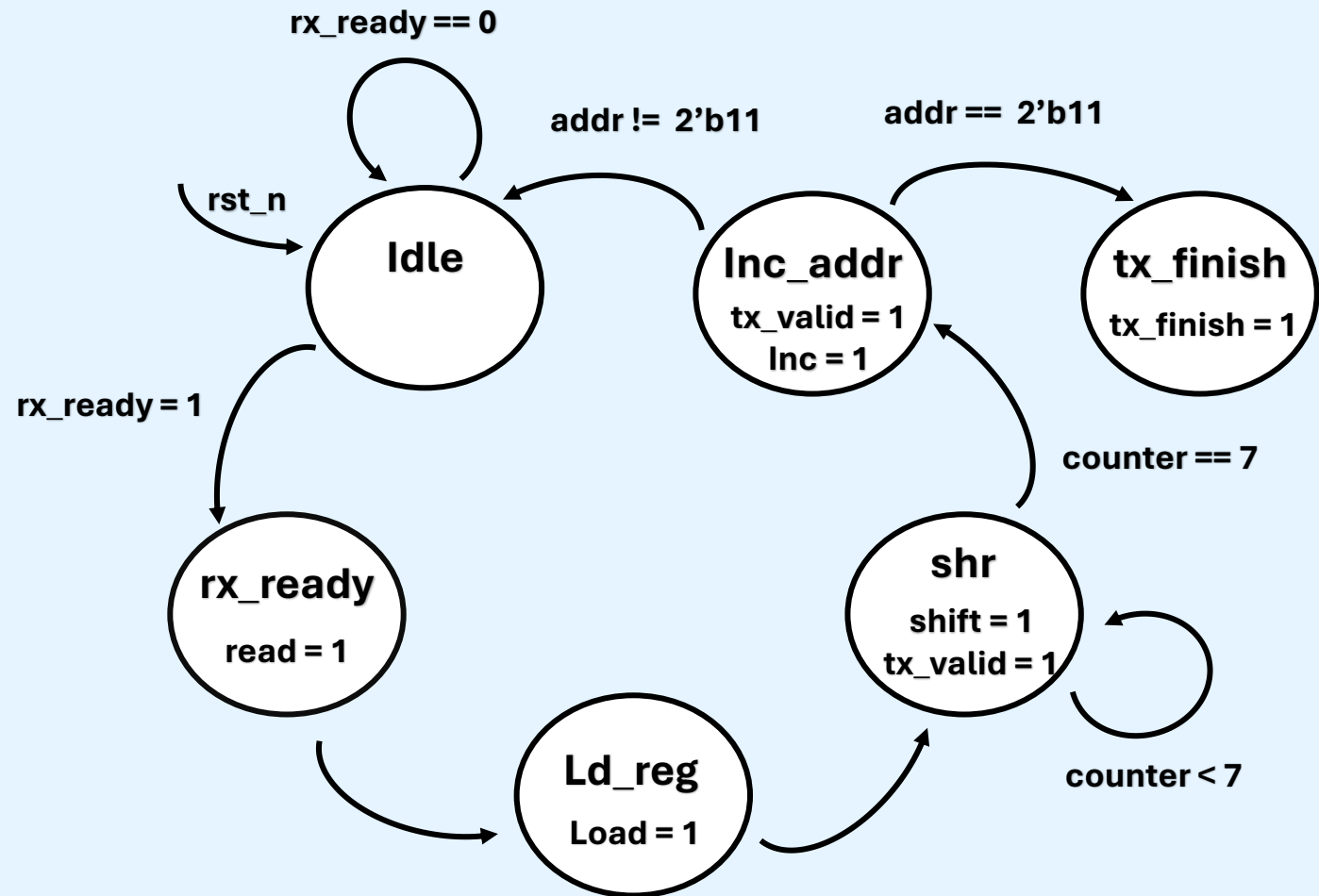

RX Block


I/O definition

 

name	I/O	Description
clk	I	50MHz
rst_n	I	active-low
tx_valid	I	Data on the tx_data wire is valid
tx_data	I	Serial data
rx_ready	O	Rx block is ready to receive data
rx_finish	O	All data is received

RX Block

Architecture

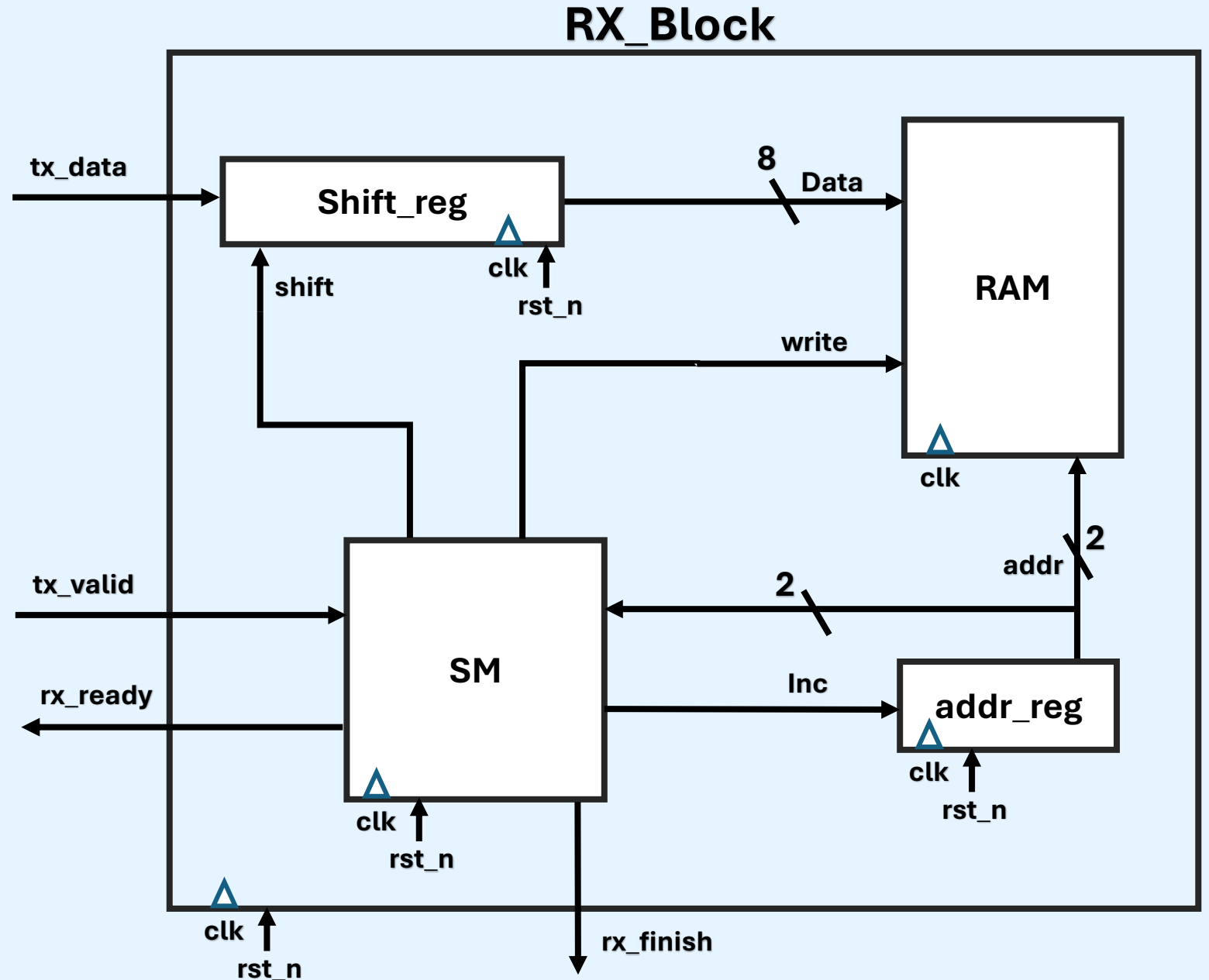

RX Block

State Machine

