 


Register


Spec



Name	Direction	Width	Description
clk	Input	1 bit	Clock signal (rising edge triggered)
reset_n	Input	1 bit	Active-low asynchronous reset
load	Input	1 bit	Load enable signal
inc	Input	1 bit	Increment enable signal
rotate_right	Input	1 bit	Rotate-right enable signal
D	Input	8 bits	Input data for load
Q	Output	8 bits	Current value of the register

Register

Functional Behavior

 

- The register is triggered on the **rising edge of clk**, unless **asynchronously reset**.
- The register supports **four main operations with the following Priority** (highest to lowest):
 1. **Asynchronous reset** (if $\text{reset_n} == 0$) \rightarrow Clear Q to 8'b0
 2. **Load** ($\text{load} == 1$) \rightarrow Load data from input D to output Q
 3. **Increment** ($\text{inc} == 1$) \rightarrow Increment Q by 1
 4. **Rotate Right** ($\text{rotate_right} == 1$) \rightarrow Circular right shift of Q by 1 bit
- **NOTE:** If No control active \rightarrow Hold previous value Only